

# Digital Integrated Circuits

## Homework#5 2024.11.20 (Due: 11.27 17:30 ED520)

Using 32nm technology with  $V_{DD} = 0.9V$ ,  $L = 32nm$ , medium  $V_t$  CMOS process.

Rise time and fall time of input signals are 0.02ns (0V-0.9V)

32nm tech. path: /RAID2/COURSE/dic/dicTA01/DIC\_2024\_Fall/bulk\_32nm.l

- (1) A 6T SRAM is shown in Fig. 1. Design the transistor widths for the SRAM to ensure proper functionality during both read and write operations. (20%)  
Generate the read and write operation curves for your SRAM cell, similar to those shown in Fig.2. (20%)
- (2) Determine the butterfly curve and the quiescent Static Noise Margin ( $SVM_{hold}$ ) of your SRAM cell in TT corners. (20%) Determine the butterfly curve and the read Static Noise Margin ( $SVM_{read}$ ) of your SRAM cell TT corners. (20%)
- (3) Design a 6T SRAM cell array under TT corner as shown in Fig. 3. Set the initial value of  $A=0$  and  $A\_b=1$  in  $SRAM_0$ . Set the initial value of  $A=1$  and  $A\_b=0$  in  $SRAM_1 \sim SRAM_{64}$ . Perform a proper read operation ( $W_0 \sim W_{63}=0$ ,  $\phi=0 \rightarrow \phi=1 \rightarrow W_0=1$ ) for  $SRAM_0$ . Generate the read operation curve and discuss the result to that of (1). What makes the difference? (20%)

 


Fig. 1. 6T SRAM Cell

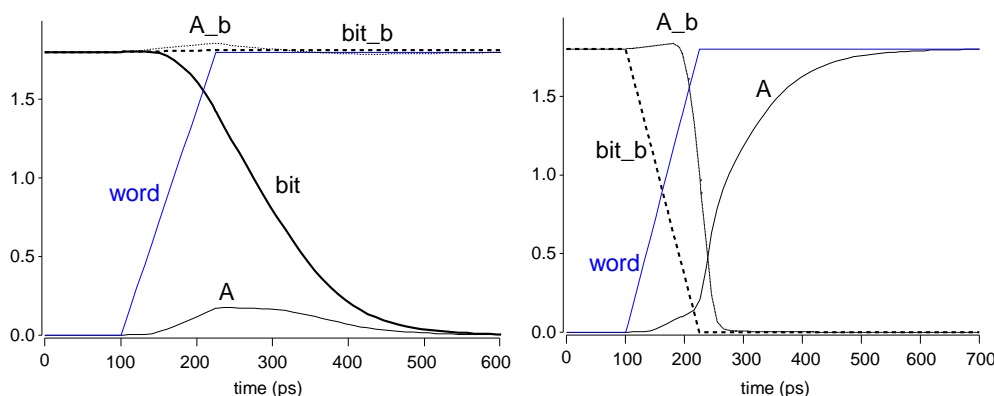


Fig. 2. Read and Write operation of the SRAM cell

 


Fig. 3 6T SRAM cell array