


Digital Integrated Circuits

#Homework 2 2024.10.11 (Due: 10.18 15:30 ED520)

Given $V_{DD}=0.8V$, $W_{min}=64nm$, $L_{min}=32nm$ with resolution of 1nm; Use Low V_t CMOS in this homework. Please submit your SPICE to E3.

 (1) Layout (40%)

- Draw the circuit schematic of the attached layout (a) and (b). The signal name each node shall be marked at the schematic. **Explain** which circuit has higher speed. (20%)
- Indicate the W/L ratio of each transistors in both (a) and (b) and A_D , A_S in terms of λ . (10%)
- Mark the design rules in (a) and (b) that determine the width of this layout. (10%)



(2) Timing and Power Analysis (60%)

- Design a two inputs NAND logic gate as shown in the following figure such that it has the logic threshold of $0.45 \cdot V_{DD}$ (when two inputs have the same voltage). Indicate the W/L of PMOS and NMOS and show the SPICE simulation results of VTC. (15%)
- Run SPICE to get the followings: (25%)
 - output capacitances and input capacitance of the NAND circuit.
 - Leakage power dissipation when $V_{in} = \text{logic 1}$, and $V_{out} = \text{logic 0}$.
 - Leakage power dissipation when $V_{in} = \text{logic 0}$, and $V_{out} = \text{logic 1}$.
- Do the timing analysis of the NAND circuit which has a fanout of two NANDs. Input signal is a pulse waveform with duration of 2ns (with $t_r = t_f = 0.4ns$ defined as 0%-100%, duty = 0.5) Run two cases by using SPICE (5ns) to get the timing (t_{df} and t_{dr}) and power waveform: (20%)
 - $A=1$ and B changes from 0 to 1.
 - $B=1$ and A changes from 0 to 1

List in table form with the t_{df} , t_{dr} , average power and peak power of the NAND circuits.

 


Fig. 2: Perfectly Symmetric 2-input NAND gate