

# Digital Integrated Circuits

## Homework#4 2024.11.06 (Due: 11.13 17:30 ED520)

Using 7nm FinFET devices with  $V_{DD} = 0.8V$ , FF process corner and medium  $V_t$  CMOS process. Rise time and fall time of input signals and clock are 0.02ns (0V-0.8V)

7nm tech. path: /RAID2/COURSE/dic/dicTA01/DIC\_2024\_Fall/7nm\_files

A 4-bit ripple carry adder shown in Fig. 1 is designed with fully complementary static logic gate of full adder (FA). Input signals are  $A[3:0]$ ,  $B[3:0]$ , and  $C_{in}$ . Outputs are  $SUM[3:0]$  and  $C_{out}$ .

- (1) Try to design the fastest adder when each input signal is driven by one unit size inverter. For the output loads, 5 unit size inverters are used for each output signal. First, show your block diagrams in terms of the 1-bit FA. Second, show the circuit schematic of the FA. Use logic effort concepts (do not have to write down the procedure) to design **transistor widths**. **Describe your design concept.** (40%)
- (2) Based on the design of (1), run SPICE to find the propagation delay (As shown in Fig. 2, with pattern from  **$IA[3:0] = 4'b1111$ ,  $IB[3:0] = 4'b0000$ ,  $IC_{in} = 1'b1$**  to  **$IA[3:0] = 4'b1111$ ,  $IB[3:0] = 4'b0000$ ,  $IC_{in} = 1'b0$** ). Determine the maximum propagation delay of the Ripple Carry Adder (exclude the load inverters). (20%)
- (3) Run SPICE of the ripple carry adder with each output load equals to 4 unit size inverter. Determine the **average, peak, and leakage** power dissipation and energy per bit, respectively when simulating at the working frequency in (2). (20%)
- (4) Add pipelining stages as shown in Fig. 4 into the 4-bit ripple carry adder, with the D register given in Fig. 3. Run SPICE to find the propagation delay time (with pattern from  **$IA[3:0] = 4'b0000$ ,  $IB[3:0] = 4'b1111$ ,  $IC_{in} = 1'b0$**  to  **$IA[3:0] = 4'b0000$ ,  $IB[3:0] = 4'b1111$ ,  $IC_{in} = 1'b1$** ) between pipelining stages to determine the **maximum working frequency** of the clock.

 


Fig. 1. Ripple Carry Adder

